

## **Four basic units of electricity**

1. **Voltage (V)** → Variable: *V*, Unit: **volt (V)**
2. **Current (I)** → Variable: *I*, Unit: **ampere (A)**
3. **Resistance (R)** → Variable: *R*, Unit: **ohm ( $\Omega$ )**
4. **Power (P)** → Variable: *P*, Unit: **watt (W)**

## **B. Equation for Ohm's Law**

$$V = I \times R \quad V = I \times R \quad R = V \div I$$

## **C. Rearranged Ohm's Law equations**

- To solve for current:  $I = \frac{V}{R}$
- To solve for resistance:  $R = \frac{V}{I}$

## **D. Power equations**

Power is  $P = V \times I$ . Rearranging with Ohm's Law gives:

- $P = V \times I$
- Substitute  $V = I \times R$ :  
 $P = I^2 \times R$
- Substitute  $I = \frac{V}{R}$ :  
 $P = \frac{V^2}{R}$

## **E. Yellow wire problem**

Given:

- $V = 12 \text{ V}$
- $P = 60 \text{ W}$
- Formula:  $P = V \times I$   
 $I = \frac{P}{V} = \frac{60}{12} = 5 \text{ A}$

**Answer: 5 A**

### **F. Orange wire problem**

Given:

- $V = 3.3 \text{ V}$
- $R = 0.25 \text{ }\Omega$
- Formula:  $P = \frac{V^2}{R}$   
 $P = \frac{3.3^2}{0.25} = 43.56 \text{ W}$

**Answer: 43.56 W**

### **G. Power supply wire problem**

Given:

- $P = 120 \text{ W}$
- $I = 24 \text{ A}$
- Formula:  $P = V \times I$

$$V = \frac{P}{I} = \frac{120}{24} = 5 \text{ V}$$

**Answer: 5 V**